Designing SCA

1. Desired behaviour

$$0 \text{ V to } 2.5 \text{ V} \rightarrow -10 \text{ V to } 10 \text{ V}$$

2. SCA Transfer Equation

$$V_{out} = mx + b = \frac{(10 V) - (-10 V)}{(2.5 V) - (0 V)} \cdot V_{in} + b = 8 \cdot V_{in} + b$$

$$(0 V, -10 V) : -10 V = 8(0 V) + b \qquad \therefore b = -10 V$$

$$V_{out} = 8 \cdot V_{in} + (-10 V)$$

3. Implementation

$$V_{out} = \frac{R_f}{R_i} \cdot V_{in} - \frac{R_f}{R_h} \cdot (2.5006 \, V^*)$$

*I will be using $V_{ref} = V_{max} + V_{LSB} = 2.5006103515625 \, V$ for V_{bias}

Let
$$R_f = 100 \, k\Omega$$

$$\frac{100 \, k\Omega}{R_i} = 8 \qquad \therefore R_i = 12.5 \, k\Omega$$

$$-\frac{100 \, k\Omega}{R_h} \cdot (2.5006 \, V) = -10 \, V \qquad \therefore R_b = 25.006 \, k\Omega$$

