X-Axis

1. Desired Behaviour

-kg to kg
$$\rightarrow$$
 0 V to V_R

2. Transducer Transfer Equation

$$V_{out i} = S \cdot a_i + V_b$$
$$a_i = \frac{V_{out i} - V_b}{S}$$

3. SCA Transfer Equation

$$V_{ADC\ i} = mx + b = \frac{V_R - 0\ V}{kg - (-kg)} \cdot a_i + \frac{V_R}{2} = \frac{V_R}{2kg} \cdot a_i + \frac{V_R}{2}$$

$$V_{ADC\,i} = \frac{V_R}{2kg} \cdot \frac{V_{out\,i} - V_b}{S} + \frac{V_R}{2} = \left(\frac{V_R}{2kg \cdot S}\right) \cdot V_{out\,i} + \left(\frac{V_R}{2} - \frac{V_R \cdot V_b}{2kg \cdot S}\right)$$

Where
$$k = 1$$
, $V_R = 2.5 V$, $S = 420 mV/g$, $V_b = \frac{V_{cc}}{2} = \frac{3.3 V}{2} = 1.65 V$

$$V_{ADCi} = (2.976190) \cdot V_{outi} - 3.660714 V$$

4. Implementation

$$V_{ADC\ i} = \left(\frac{R_f}{R_i}\right) \cdot V_{out\ i} - \left(\frac{R_f}{R_b}\right) \cdot V_{bias}$$

Choose $V_{bias} = 3.3 V$ from MSP430

Let
$$R_f = 100 k\Omega$$

$$\frac{100 \, k\Omega}{R_i} = 2.976190 \qquad \therefore R_i = 33.6 \, k\Omega$$

$$-\frac{100 \, k\Omega}{R_b} \cdot (3.3 \, V) = -3.660714 \, V \qquad \therefore R_b = 90.146341 \, k\Omega$$

Y-Axis

1. Desired Behaviour

0 g to kg
$$\rightarrow$$
 0 V to V_R

2. Transducer Transfer Equation

$$V_{out i} = S \cdot a_i + V_b$$
$$a_i = \frac{V_{out i} - V_b}{S}$$

3. SCA Transfer Equation

$$V_{ADC\ i} = mx + b = \frac{V_R - 0\ V}{k\,q - 0\ q} \cdot a_i + \frac{V_R}{2} = \frac{V_R}{k\,q} \cdot a_i + \frac{V_R}{2}$$

$$V_{ADC\,i} = \frac{V_R}{kg} \cdot \frac{V_{out\,i} - V_b}{S} + \frac{V_R}{2} = \left(\frac{V_R}{kg \cdot S}\right) \cdot V_{out\,i} + \left(\frac{V_R}{2} - \frac{V_R \cdot V_b}{kg \cdot S}\right)$$

Where
$$k = 1$$
, $V_R = 2.5 V$, $S = 420 mV/g$, $V_b = \frac{V_{cc}}{2} = \frac{3.3 V}{2} = 1.65 V$

$$V_{ADCi} = (5.952381) \cdot V_{outi} - (8.571429 V)$$

4. Implementation

$$V_{ADC\ i} = \left(\frac{R_f}{R_i}\right) \cdot V_{out\ i} - \left(\frac{R_f}{R_b}\right) \cdot V_{bias}$$

Choose $V_{bias} = 3.3 V$ from MSP430

Let
$$R_f = 100 k\Omega$$

$$\frac{100 \, k\Omega}{R_i} = 5.952381 \qquad \therefore R_i = 16.8 \, k\Omega$$

$$-\frac{100 \ k\Omega}{R_b} \cdot (3.3 \ V) = -8.571429 \ V \qquad \therefore R_b = 38.5 \ k\Omega$$

